


# **ENGG2020 Digital Logic and Systems**

## **Chapter 6: Sequential Logic Circuits**

The Chinese University of Hong Kong
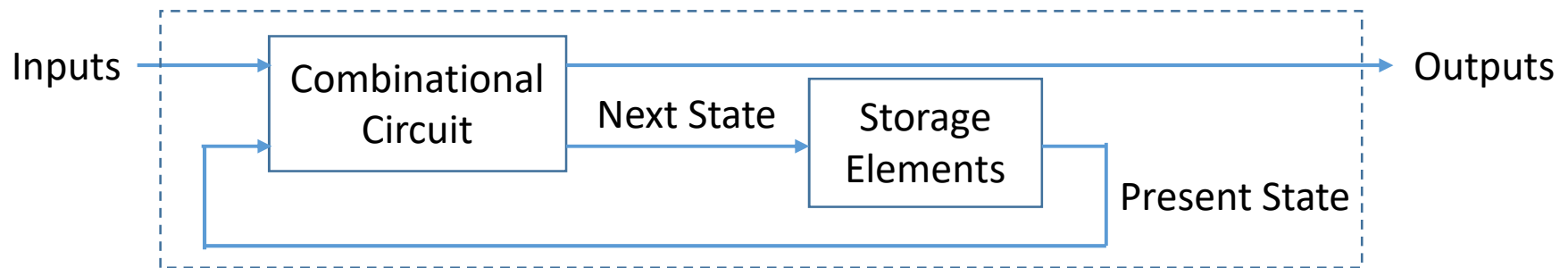
# Sequential Logic Circuits


- The outputs at any instant of time depend upon the present inputs as well as past inputs/outputs i.e. there are elements used to store past information
- Finite State Machine (FSM) can be used to design the sequential logic circuits



# Finite State Machines

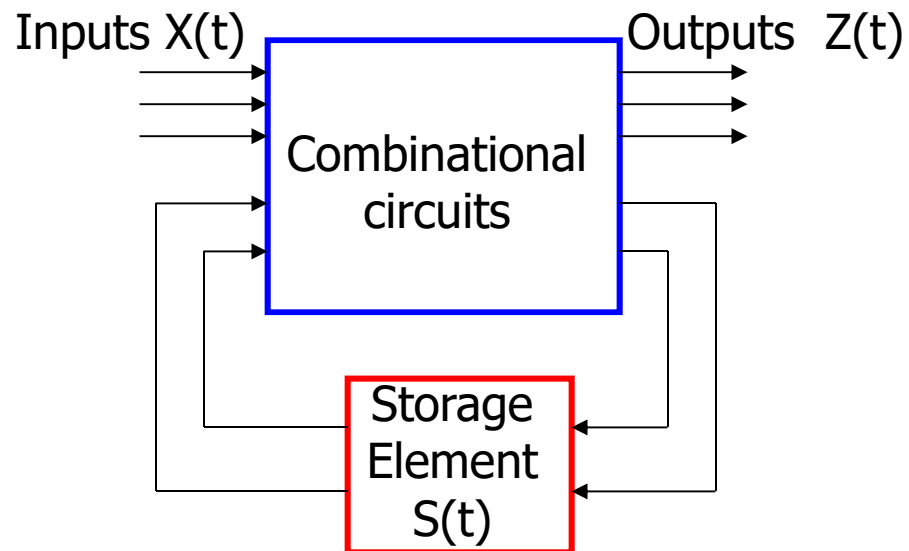
## Mealy Machine Model

- Outputs are a function of inputs and states



## Moore Machine Model

- Outputs are a function of states only

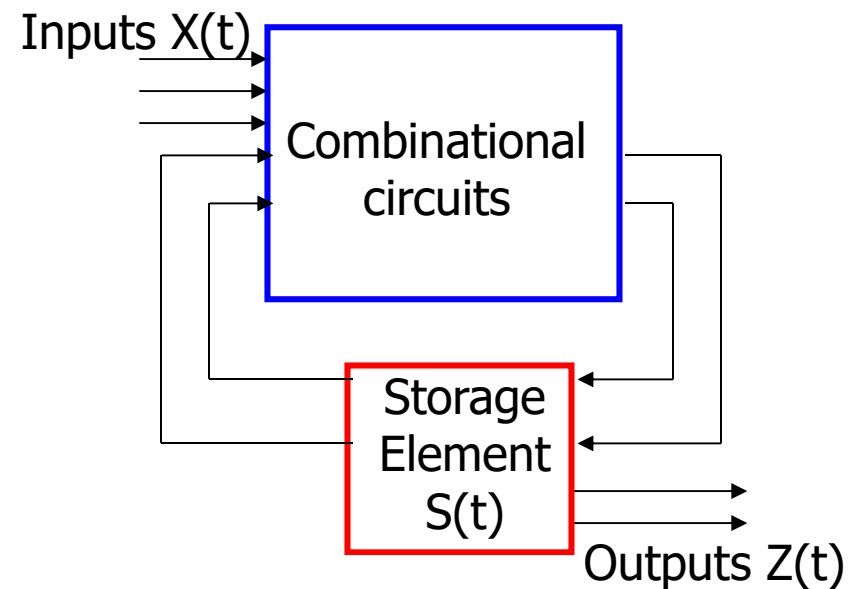

# Finite State Machines (2)

- Each FSM is defined by a list of its states, and the triggering condition for each transition
  - The machine is in only one state at a time
  - Current state – the state it is in at any given time
  - Transition – change from one state to another when initiated by a triggering event or condition
- State Table shows what state a FSM will move to, based on the current state and other inputs
- State Diagram is a graphic representation of the state table

# State Table

Present state	Next state		Output Z	
	X=0	X=1	X=0	X=1
A	A	B	0	0
B	A	C	0	0
C	D	C	0	0
D	A	B	0	1

State table


Present state	Next state		Output Z	
	X=0	X=1	X=0	X=1
00	00	01	0	0
01	00	11	0	0
11	10	11	0	0
10	00	01	0	1

State names replaced by binary codes  
(A=00; B=01; C=11; D=10)

# State Diagram


## Mealy Machine Model

- Label input/output along each arc

 
 
## Moore Machine Model


- Label input along each arc
- Label output inside the circle




# State Diagram Examples

## Mealy Machine Model

### Example 1

 


### Example 2

 


## Moore Machine Model

### Example 1

 

### Example 2

 

# Design a Sequential Circuit

Step 1: Obtain either the state diagram or the state table

Step 2: Make a Next State Truth Table

Step 3: Pick Flip-Flop type for each bit and add Flip-Flop inputs to the Next State Truth Table

Step 4: Solve equations for Flip-Flop inputs

Step 5: Solve equations for Flip-Flop outputs

Step 6: Implement the circuit



# Excitation Table for Flip-Flops

- The excitation table rearranges the order of true table (characteristic table) of the flip-flops in order to list the required inputs for a given change of state
- The inputs of the excitation table are  $Q_n$  and  $Q_{n+1}$  while the output of the excitation table is the flip-flop's control bits

# Excitation Table for Flip-Flops (2)

- D Flip-Flop

$Q_n$	$Q_{n+1}$	D
0	0	0
0	1	1
1	0	0
1	1	1

- T Flip-Flop

$Q_n$	$Q_{n+1}$	T
0	0	0
0	1	1
1	0	1
1	1	0

# Excitation Table for Flip-Flops (3)

- SR Flip-Flop

$Q_n$	$Q_{n+1}$	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0


- JK Flip-Flop

$Q_n$	$Q_{n+1}$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0
 
# Design with Moore Machine Example

Design a sequence recognizer to recognize 01 or 10

Step 1: Get the state diagram or state table



# Design with Moore Machine Example (2)

Step 2a: Make a Next State Truth Table

$\overline{\text{Reset}}$	Current State	Input	Next State	Output
0	d	d	A	0
1	A	0	B	0
1	A	1	C	0
1	B	0	B	0
1	B	1	D	0
1	C	0	E	0
1	C	1	C	0
1	D	0	E	1
1	D	1	C	1
1	E	0	B	1
1	E	1	D	1

# Design with Moore Machine Example (3)

Step 2b: Make a Next State Truth Table using Binary Code

$\overline{\text{Reset}}$	Current State $Q_2Q_1Q_0$	Input $X$	Next State $Q_2^+Q_1^+Q_0^+$	Output $Z$
0	ddd	d	000	0
1	000	0	001	0
1	000	1	010	0
1	001	0	001	0
1	001	1	011	0
1	010	0	100	0
1	010	1	010	0
1	011	0	100	1
1	011	1	010	1
1	100	0	001	1
1	100	1	011	1

# Design with Moore Machine Example (4)

Step 3: Pick Flip-Flop type for each bit and add Flip-Flop inputs to the Next State Truth Table

$\overline{\text{Reset}}$	Current State $Q_2Q_1Q_0$	Input $X$	Next State $Q_2^+Q_1^+Q_0^+$	Flip-Flop Input $D_2D_1D_0$	Output $Z$
0	ddd	d	000	000	0
1	000	0	001	001	0
1	000	1	010	010	0
1	001	0	001	001	0
1	001	1	011	011	0
1	010	0	100	100	0
1	010	1	010	010	0
1	011	0	100	100	1
1	011	1	010	010	1
1	100	0	001	001	1
1	100	1	011	011	1

# Design with Moore Machine Example (5)

Step 4: Solve equations for Flip-Flop inputs

Get the equations

$$D_2 = m(4, 6) + d(10, 11, 12, 13, 14, 15)$$

$$D_1 = m(1, 3, 5, 7, 9) + d(10, 11, 12, 13, 14, 15)$$

$$D_0 = m(0, 2, 3, 8, 9) + d(10, 11, 12, 13, 14, 15)$$

Simplify the equations

$$D_2 = Q_1 \bar{X}$$

$$D_1 = X$$

$$D_0 = \overline{Q_1} \bar{X} + \overline{Q_1} Q_0 + Q_2$$



# Design with Moore Machine Example (6)

Step 5: Solve equations for Flip-Flop outputs

As this is a Moore Machine, the output does not depend on the inputs, so  $X$  can be neglected

Get the equation


$$Z = m(3, 4) + d(5, 6, 7)$$

Simplify the equations

$$Z = Q_1 Q_0 + Q_2$$

# Design with Moore Machine Example (7)

## Step 6: Implement the circuit

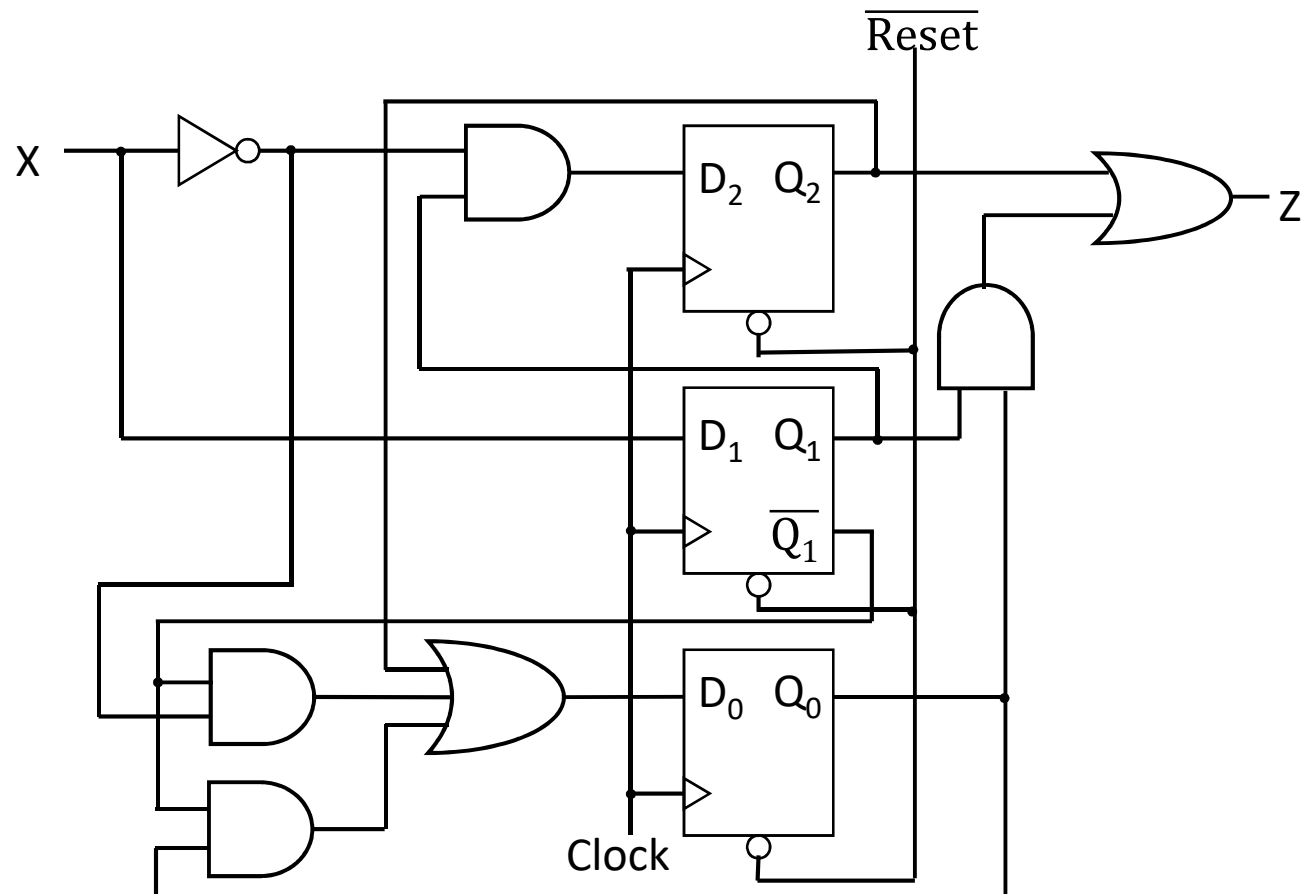


# Synchronous Counter

- All the clock inputs tied together so that each flip-flop changes state at the same time
  - Propagation for the whole counter is the same as one flip-flop
- Each flip-flop must be steered by using the JK input → change to its proper state when the next clock comes along
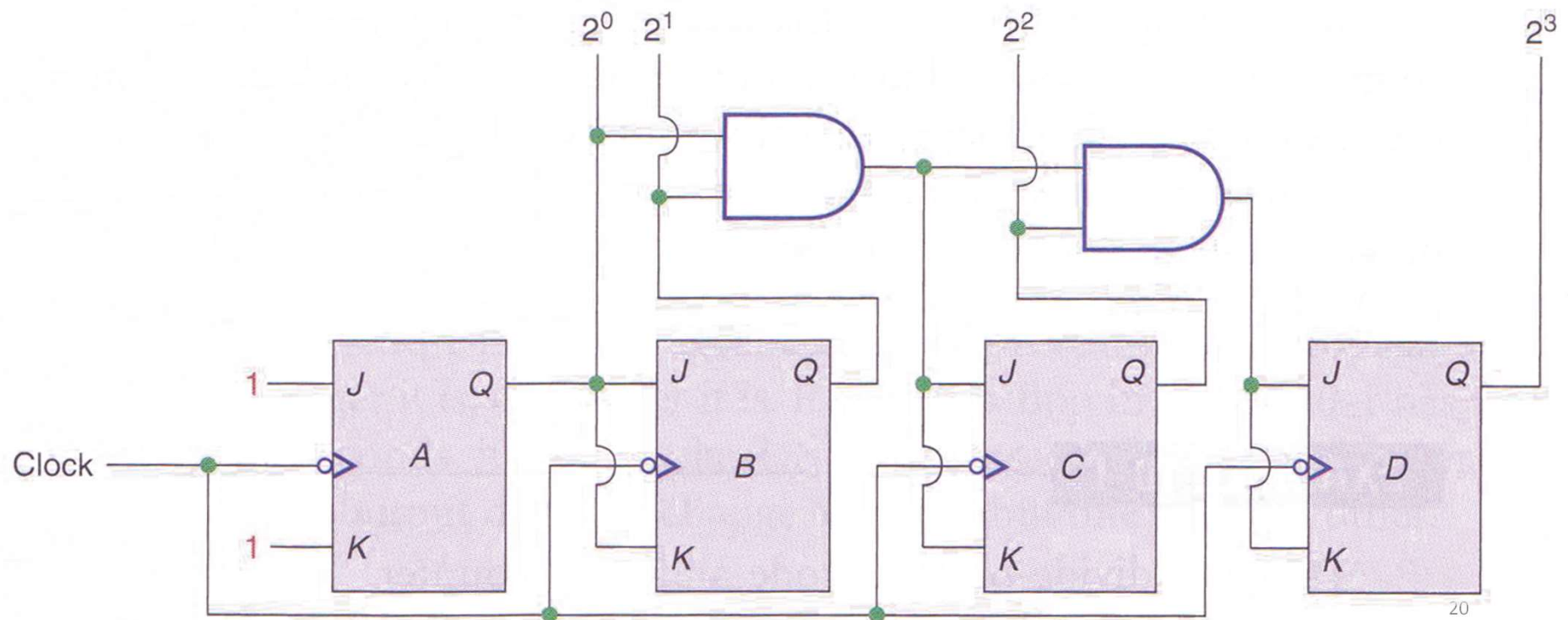
# Synchronous Counter Example

- Same as divide-by-16 ripple counter, but this is much faster



# Design a Divide-By-5 Synchronous Counter

Step 1: Obtain either the state diagram or the state table

Step 2: Make a Next State Truth Table

Step 3: Pick Flip-Flop type for each bit and add Flip-Flop inputs to the Next State Truth Table


Step 4: Solve equations for Flip-Flop inputs

Step 5: Solve equations for Flip-Flop outputs

Step 6: Implement the circuit
 
# Design a Divide-By-5 Synchronous Counter – Step 1

Step 1: Obtain either the state diagram or the state table



# Design a Divide-By-5 Synchronous Counter – Step 2

Step 2: Make a Next State Truth Table

Current State $Q_2Q_1Q_0$	Next State $Q_2^+Q_1^+Q_0^+$	Output $Z_2Z_1Z_0$
000	001	001
001	010	010
010	011	011
011	100	100
100	000	000

# Design a Divide-By-5 Synchronous Counter – Step 3

Step 3: Pick Flip-Flop type for each bit and add Flip-Flop inputs to the Next State Truth Table

Current State $Q_2Q_1Q_0$	Next State $Q_2^+Q_1^+Q_0^+$	$J_2$	$K_2$	$J_1$	$K_1$	$J_0$	$K_0$	Output $Z_2Z_1Z_0$
000	001	0	X	0	X	1	X	001
001	010	0	X	1	X	X	1	010
010	011	0	X	X	0	1	X	011
011	100	1	X	X	1	X	1	100
100	000	X	1	0	X	0	X	000



# Design a Divide-By-5 Synchronous Counter – Step 4

Step 4: Solve equations for Flip-Flop inputs

Current State $Q_2Q_1Q_0$	Next State $Q_2^+Q_1^+Q_0^+$	$J_2$	$K_2$	$J_1$	$K_1$	$J_0$	$K_0$
000	001	0	x	0	x	1	x
001	010	0	x	1	x	x	1
010	011	0	x	x	0	1	x
011	100	1	x	x	1	x	1
100	000	x	1	0	x	0	x

$$J_2 = m(3) + d(4, 5, 6, 7)$$

$$K_2 = m(4) + d(0, 1, 2, 3, 5, 6, 7)$$

$$J_1 = m(1) + d(2, 3, 5, 6, 7)$$

$$K_1 = m(3) + d(0, 1, 4, 5, 6, 7)$$

$$J_0 = m(0, 2) + d(1, 3, 5, 6, 7)$$

$$K_0 = m(1, 3) + d(0, 2, 4, 5, 6, 7)$$

# Design a Divide-By-5 Synchronous Counter – Step 4 (2)

Q <sub>2</sub> Q <sub>1</sub>		00	01	11	10
Q <sub>0</sub>	0	0 X	2 X	6 X	4 X
	1	1 X	3 1	7 X	5 X

$$J_2 = Q_1 Q_0$$

Q <sub>2</sub> Q <sub>1</sub>		00	01	11	10
Q <sub>0</sub>	0	0 X	2 X	6 X	4 1
	1	1 X	3 X	7 X	5 X

$$K_2 = 1$$

# Design a Divide-By-5 Synchronous Counter – Step 4 (3)

Q <sub>2</sub> Q <sub>1</sub>					
Q <sub>0</sub>		00	01	11	10
	0	0	2 X	6 X	4
	1	1 1	3 X	7 X	5 X

$$J_1 = Q_0$$

Q <sub>2</sub> Q <sub>1</sub>					
Q <sub>0</sub>		00	01	11	10
	0	0 X	2	6 X	4 X
	1	1 X	3 1	7 X	5 X

$$K_1 = Q_0$$

# Design a Divide-By-5 Synchronous Counter – Step 4 (4)

Q <sub>2</sub> Q <sub>1</sub>		00	01	11	10
Q <sub>0</sub>	0	0 1	2 1	6 X	4 
	1	1 X	3 X	7 X	5 X

$$J_0 = \overline{Q_2}$$

Q <sub>2</sub> Q <sub>1</sub>		00	01	11	10
Q <sub>0</sub>	0	0 X	2 X	6 X	4 X
	1	1 1	3 1	7 X	5 X

$$K_0 = 1$$

# Design a Divide-By-5 Synchronous Counter – Step 5

Step 5: Solve equations for Flip-Flop outputs

As the output is exact the same as the next state value, the output of all flip-flops will be the circuit's output

$$Z_2 = Q_2^+$$

$$Z_1 = Q_1^+$$

$$Z_0 = Q_0^+$$

# Design a Divide-By-5 Synchronous Counter – Step 6

Step 6: Implement the circuit

